```
% Design exercise
clear ; clc ;
rect2polard = @(z) [abs(z) rad2deg(angle(z))];
polard2rect = @(z) z(1)*exp(1j*deg2rad(z(2)));
get_gamma = @(Z) (Z-50)/(Z+50)
get_gamma = function_handle with value:
   @(Z)(Z-50)/(Z+50)
get_Z = @(gamma) 50*(1+gamma)/(1-gamma)
get_Z = function_handle with value:
   @(gamma)50*(1+gamma)/(1-gamma)
Z0 = 50;
%%% From stability.dds @ 2GHz: RStabCkt..Sopt = 0.490 / 104.992
S_{opt} = polard2rect([ 0.444 98.626])
S_{opt} = -0.0666 + 0.4390i
f = 2e9;
w = 2*pi*f;
gamma_in = conj(S_opt)
gamma in = -0.0666 - 0.4390i
Zin = get_Z(gamma_in)
Zin = 30.1756 - 32.9979i
R_in = real(Zin);
X_{in} = (imag(Zin));
% check lumped elements matching configuration 1
XL = X_{in};
RL = R_{in};
B_Lin = (XL - sqrt(RL/Z0)*sqrt(RL^2+XL^2-Z0*RL))/(RL^2+XL^2)
B_{Lin} = -0.0251
Lin = 1/(w*B_Lin)
```

```
X_{Cin} = 1/B_{Lin} + XL*Z0/RL - Z0/(B_{Lin}*RL)
X_{Cin} = -28.5129
Cin = 1/(w*X_Cin)
Cin = -2.7909e-12
clear XL RL
C_{in} = 2.8e-12;
L_{in} = 3.2e-9;
Z0 = 50;
Z_{Cin} = 1/(j*w*C_{in});
Z_{\text{Lin}} = (j*w*L_{\text{in}});
Z_SM = 1/(1/(Z0+Z_Cin) + 1/(Z_Lin))
Z_SM = 30.6367 + 32.9871i
gamma_S = get_gamma(Z_SM)
gamma_S = -0.0623 + 0.4346i
rect2polard(gamma_S)
ans = 1 \times 2
   0.4390
           98.1641
S11 = polard2rect([0.571 -124.400]);
S12 = polard2rect([0.087 29.260]);
S21 = polard2rect([2.871 82.700]);
S22 = polard2rect([0.707 -41.920]);
% S = [S11 S12 ; S21 S22] ;
% rect2polard(S(:))
\% gamma_S = get_gamma(25.727 + j*31.811)
% rect2polard(gamma_S)
gamma_out = S22 + (gamma_S*S21*S12)/(1-gamma_S*S11)
gamma out = 0.3962 - 0.5248i
rect2polard(gamma_out)
```

ans = 1×2

```
Z_out = get_Z(gamma_out)
Z_{out} = 44.3489 - 82.0009i
rect2polard(Z_out)
ans = 1 \times 2
  93.2254 -61.5939
L_stab = 10e-9;
R_stab = 30;
Z_stability = R_stab + j*w*L_stab
Z_{stability} = 3.0000e+01 + 1.2566e+02i
Z_{out\_stab} = 1/((1/Z_{out}) + (1/Z_{stability}))
Z_{out\_stab} = 1.3464e+02 - 3.7202e+01i
% rect2polard(Z_out_stab)
gamma_out_stab = get_gamma(Z_out_stab)
gamma_out_stab = 0.4795 - 0.1049i
rect2polard(gamma_out_stab)
ans = 1 \times 2
   0.4909 -12.3346
% check lumped elements matching configuration 1
XL = imag(Z_out_stab);
RL = real(Z_out_stab) ;
B_Lout = (XL - sqrt(RL/Z0)*sqrt(RL^2+XL^2-Z0*RL))/(RL^2+XL^2)
B_Lout = -0.0114
Lout = 1/(w*B_Lout)
Lout = -6.9719e-09
X_Cout = 1/B_Lout + XL*ZO/RL - ZO/(B_Lout*RL)
X_{\text{cout}} = -68.8923
Cout = 1/(w*X\_Cout)
```