

CREATE OUTPUT MATCHING NETWORK: Step 1

With the input matching network in place, the output of the amplifier is matched to 50 Ohms.

1) The reflection coefficient of the complete amplifier (input matching network, device, stabilizing network) is measured, with a TLout1 at the output.

2) The length of TLout1 is swept until the real part of the amplifier's output conductance is 20 mS.

SIMULATIONS



S-PARAMETERS

S_Param
SP1
Freq=2 GHz



PARAMETER SWEEP

ParamSweep
Sweep1
SweepVar="Lout1_value"
SimInstanceName[1]="SP1"
SimInstanceName[2]=
SimInstanceName[3]=
SimInstanceName[4]=
SimInstanceName[5]=
SimInstanceName[6]=
Start=52
Stop=53
Step=0.1

S-parameter simulation is run at a single frequency (2GHz), while TLout1 length is swept.

