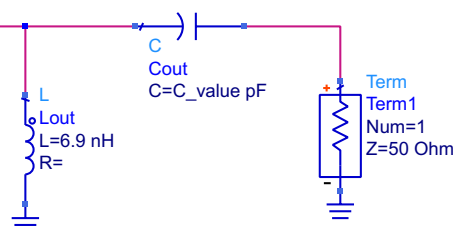


CREATE OUTPUT MATCHING NETWORK: Step 2

With the input matching network in place, the output of the amplifier is matched to 50 Ohms.

- 1) The shunt inductor is set to 6.9 nH, the value found in Match3.dsn.
- 2) The capacitance value is swept until the reactive part of the amplifier's output impedance is eliminated. (see OutputMatch.dds).



SIMULATIONS

S-PARAMETERS	PARAMETER SWEEP
--------------	-----------------

S_Param
SP1
Freq=2 GHz

S-parameter simulation is run at a single frequency (2GHz), while the capacitor value is swept.

ParamSweep
Sweep1
SweepVar="C_value"
SimInstanceName[1]="SP1"
SimInstanceName[2]=
SimInstanceName[3]=
SimInstanceName[4]=
SimInstanceName[5]=
SimInstanceName[6]=
Start=1
Stop=2
Step=0.1

VARIABLES

VAR
VAR1
C_value=0

"C_value" is defined here and set to 0. The actual values used in simulation are set in the ParamSweep component.