

## CREATE INPUT MATCHING NETWORK: Step 2

The device will be matched for minimum noise figure at 2 GHz.

- 1) The input reflection of "S1" is set to the complex conjugate of the impedance to be matched to 50 Ohms (in this case, "Opt", the optimum noise match). The inductor is set to 3.2nH, from Match1.dsn.
- 2) The capacitor is swept until the reactive part of the input impedance is eliminated (see InputMatch.dds).

### SIMULATIONS



#### S-PARAMETERS


S\_Param  
SP1  
Freq=2 GHz


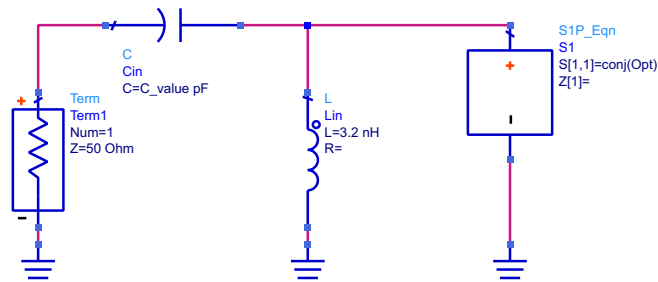
#### PARAMETER SWEEP

ParamSweep  
Sweep1  
SweepVar="C\_value"  
SimInstanceName[1]="SP1"  
SimInstanceName[2]=  
SimInstanceName[3]=  
SimInstanceName[4]=  
SimInstanceName[5]=  
SimInstanceName[6]=  
Start=2.5  
Stop=3  
Step=0.1

S-parameter simulation is run at a single frequency (2GHz), while the capacitor value is swept.



### VARIABLES

Var  
Eqn  
VAR  
VAR1  
Opt=polar(0.444,98.626)  
C\_value=0

"C\_value" is defined here and set to 0. The actual values used in simulation are set in the ParamSweep component.