

UNIVERSITY OF OULU



FACULTY OF INFORMATION TECHNOLOGY AND ELECTRICAL ENGINEERING - ITEE

ELECTRONICS DESIGN 3

DESIGN EXERCISE REPORT

Students:

- AZZAZ Aissa (Number: 2207335)

Date: January 23, 2023

1. Mirror based OTa

The two stage OpAmp to be used in the design exercise is shown in Figure ?? in which the bias circuitry is simplified.

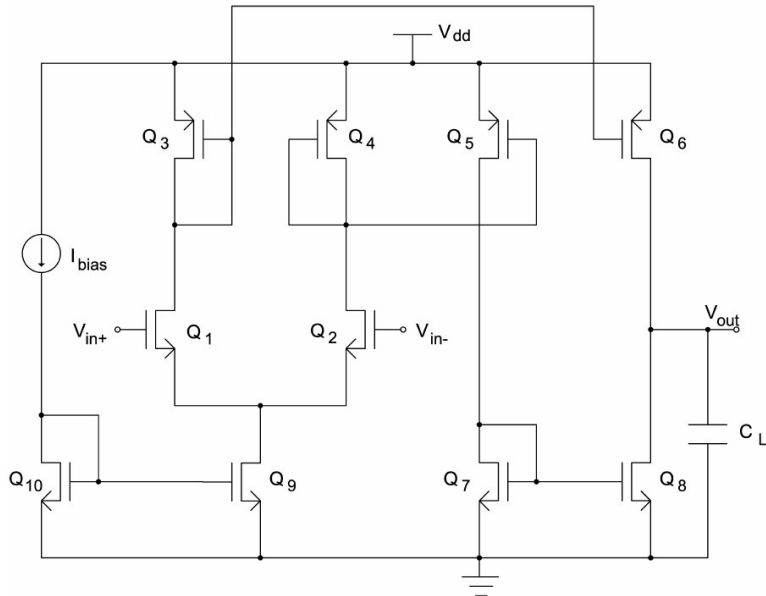


Figure 1: Mirror based OTA schematic

2. Sizing the OTA

The hand calculation of the Mirror based OTA are provided in the textbook [Analog Integrated Circuit Design, 2E] and are further explained in exercise 2.2 and the lab manual. The specifications of f_t and SR were stressed by 20% to meet the requirements, and the output and CM input ranges were increased by 200 mV for the same reason.

Figure 2 shows the OTA without the bias circuit. A constant G_m circuit is used to provide the bias current and Figure 3 shows the OTA with the bias circuit. In addition transistor were divided using the finger multiplier coefficient and dummy ones were added to prepare for the layout. Table 1 shows the results of hand calculations and the tweaking and optimization to ease the layout and match the DC operating points with the simplified bias circuit.

Table 1: The results of all the simulations

	Length (μm)	Calculated total Width (μm)	Optimized total Width (μm)	Nbr Fingers
W_1, W_2	0.4	3.95	4	4
W_3, W_4, W_5	3	3.91	4	4
W_6	3	7.81	8	8
W_7	3	4.69	4.6	2
W_8	3	9.38	9.2	4
W_9, W_{10}, W_{11}	3	3.54	3.6	6
W_{12}, W_{14}	3	3	3	2
W_{15}	3	3	12	8
R_{bias}	/	15.5 K Ω	4.4 K Ω	/
I_{bias}	/	74 μA	75 μA	/

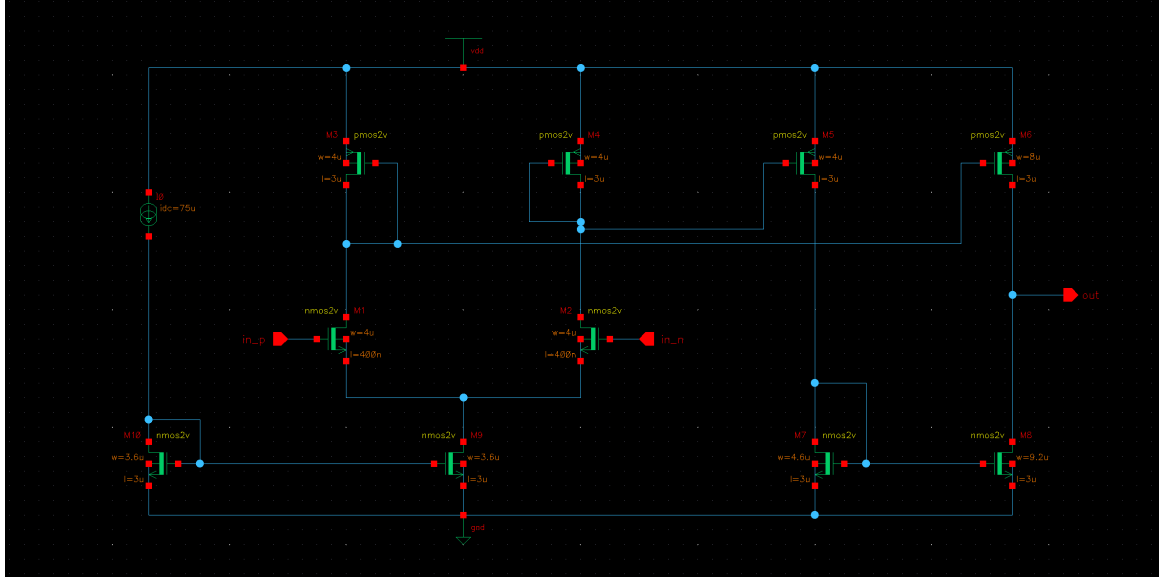


Figure 2: OTA schematic with simplified bias circuit

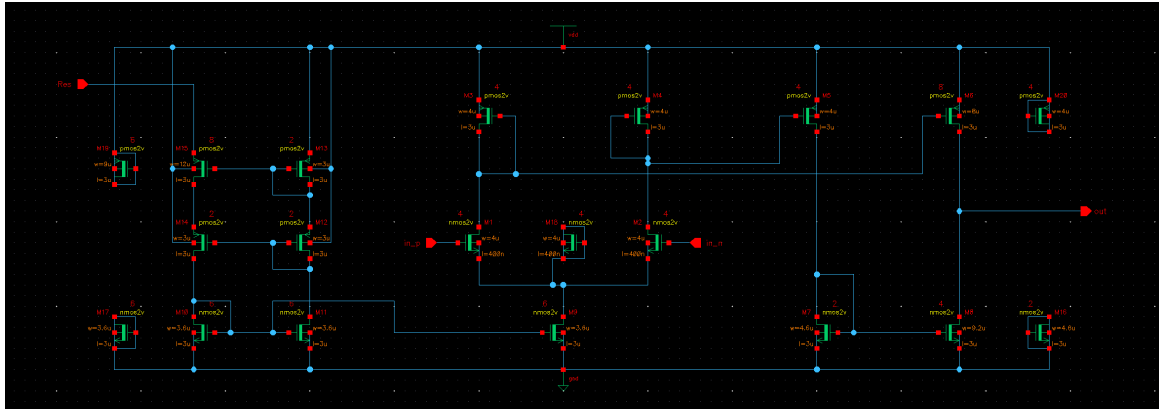


Figure 3: OTA schematic with constant G_m bias circuit

3. Schematic Simulations

In the subsections below, the different test benches and their results, Figure 4 are presented. The main results are summarized in Table 2 below.

Table 2: The results of all schematic simulations

	OTA simulation result	Figure
f_{ta}	11.56908 MHz	7
BW	123.163 kHz	7
A_0	39.48111 dB	7
PM	75.3938°	7
Slew Rate	14.334105 MV/s	12
$V_{in,CM}$ range	[1.014768 V , 2.325984 V]	11
V_{out} range	[564.0741 mV , 2.235647 V]	13

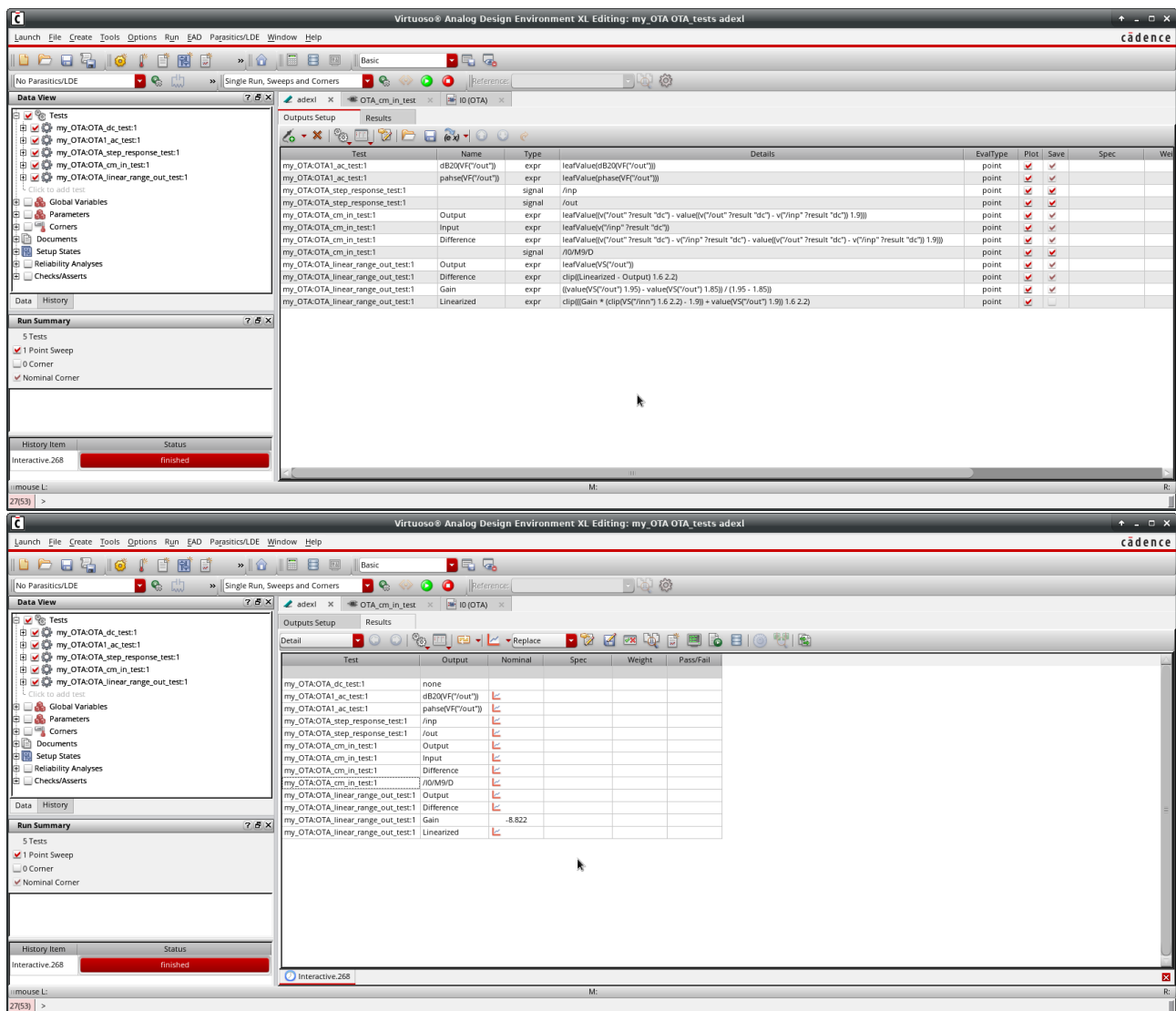


Figure 4: Tests setup and their results

3.1 DC simulation

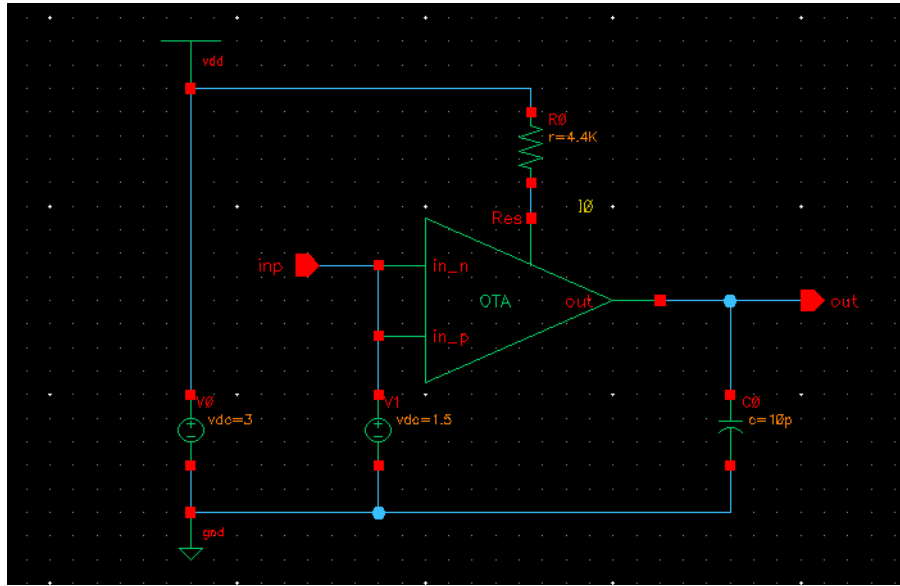


Figure 5: DC simulation test bench

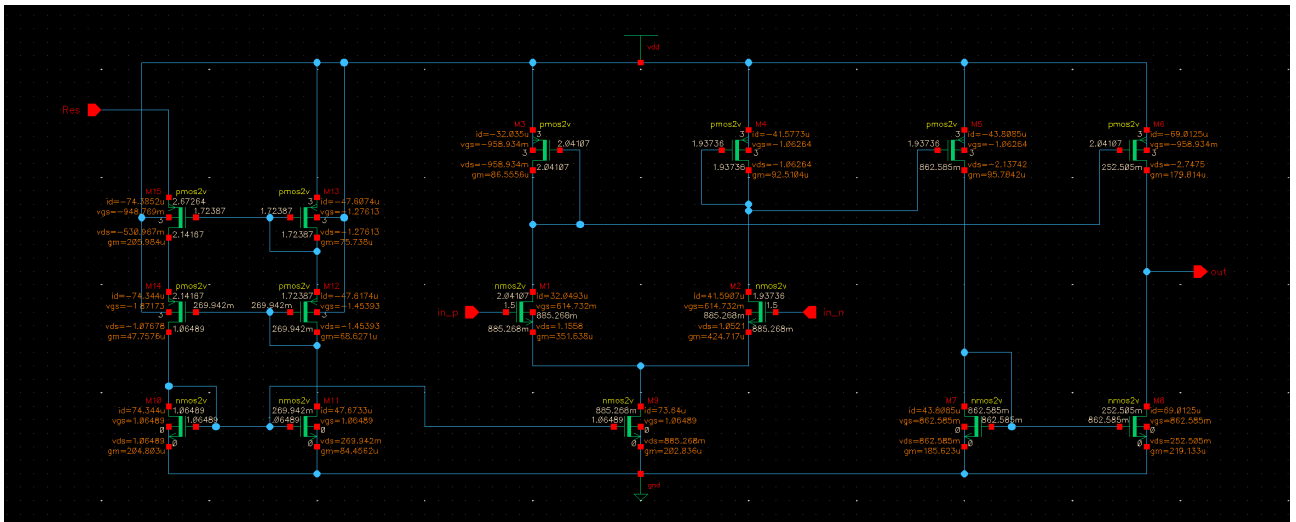


Figure 6: DC operating point of the OTA

3.2 AC Response

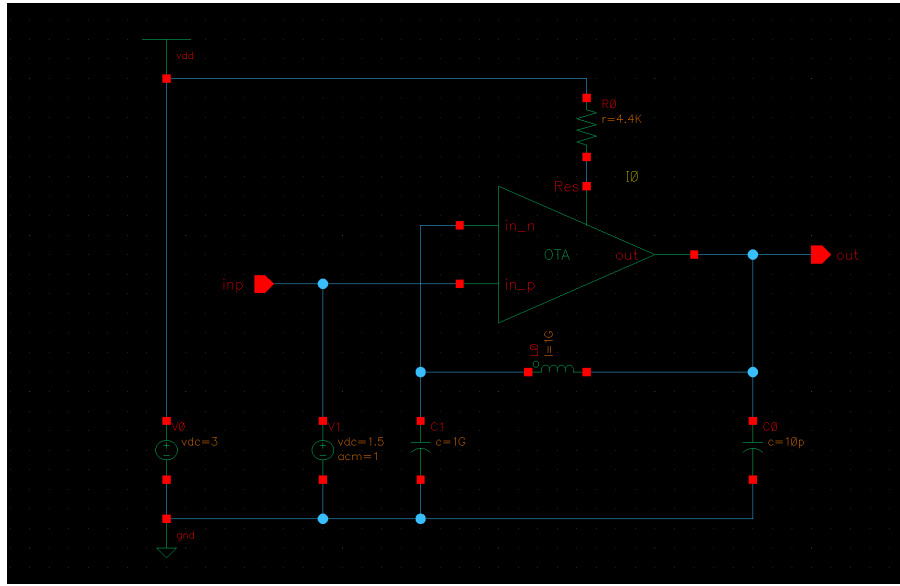


Figure 7: AC response test bench

AC Response

Name
dB20(VF("/out"))

 


Figure 8: AC response of the OTA

3.3 Step Response

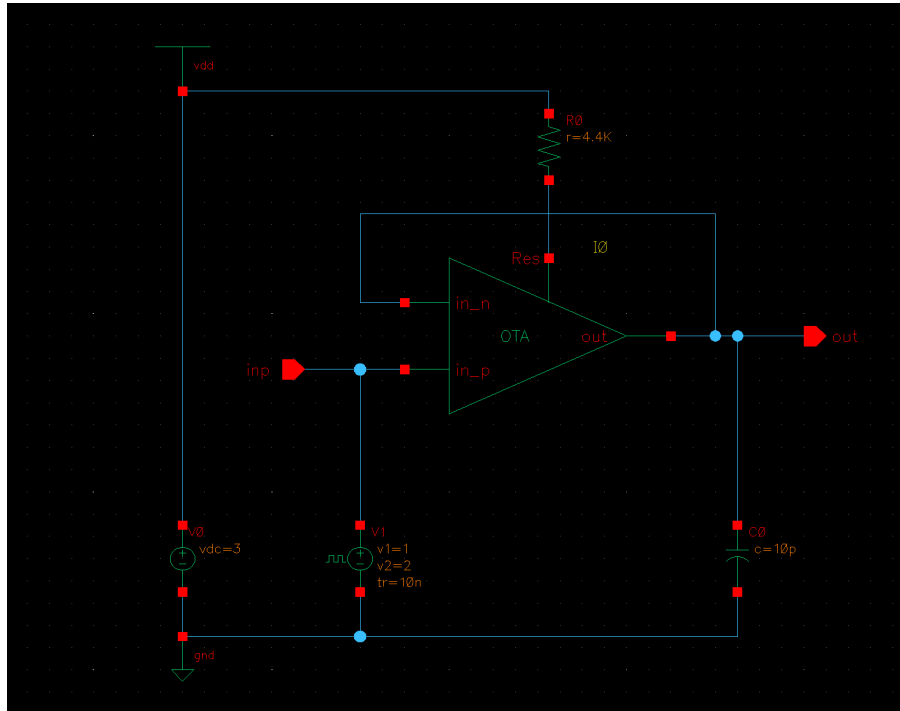


Figure 9: Step response test bench

Transient Response

 


Figure 10: Step response of the OTA

3.4 Input Common mode (CM) range


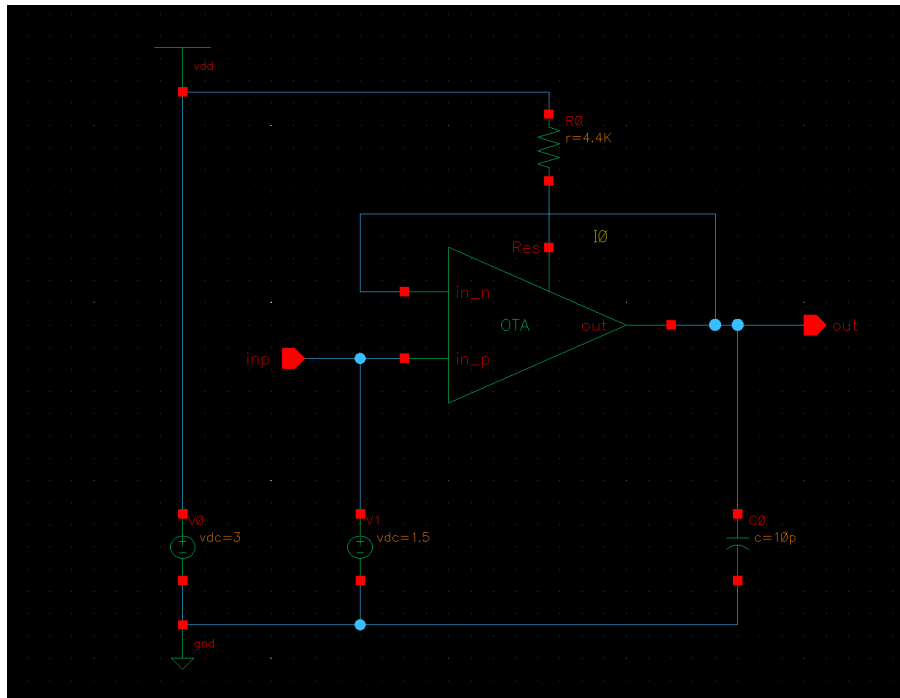


Figure 11: Input CM range test bench

DC Response

Mon Jan 23 22:49:20 2023

 

Wed Jan 11 22:12:52 2023

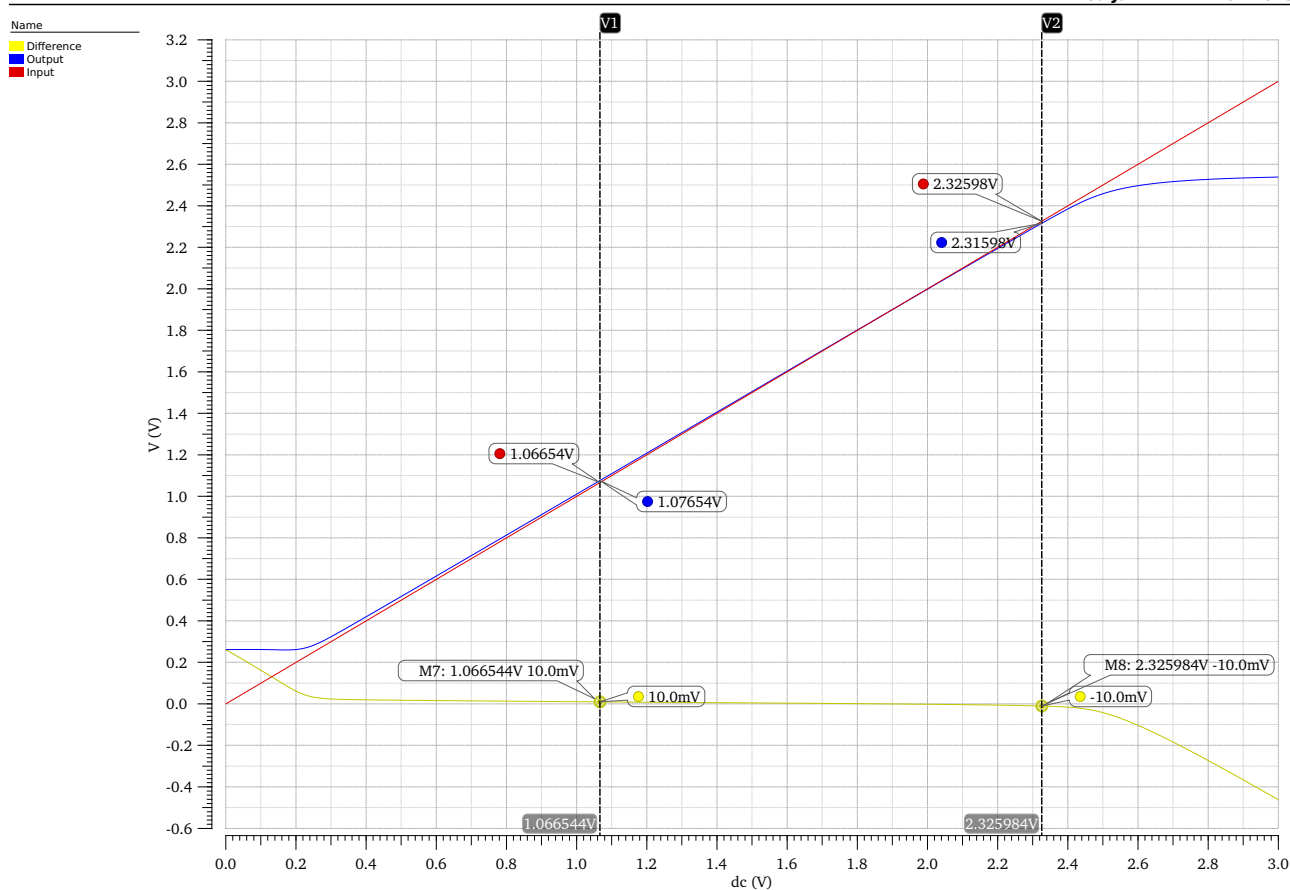


Figure 12: Minimum and maximum input CM range simulation for the OTA

3.5 Output range

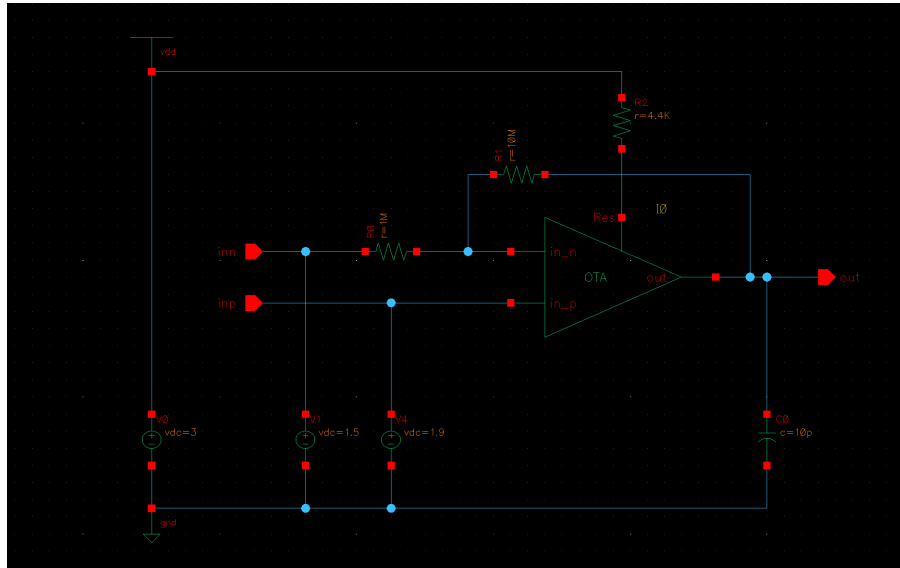


Figure 13: Output range test bench

 


Figure 14: Output range simulation for the OTA

4. The layout

The common centroid structure with mirrored elements is used as shown in Figures 15 and 16. In addition the dummy elements were distributed around each matched set of transistor. The layout passes both DRC and IVS checks as shown in Figure 17.

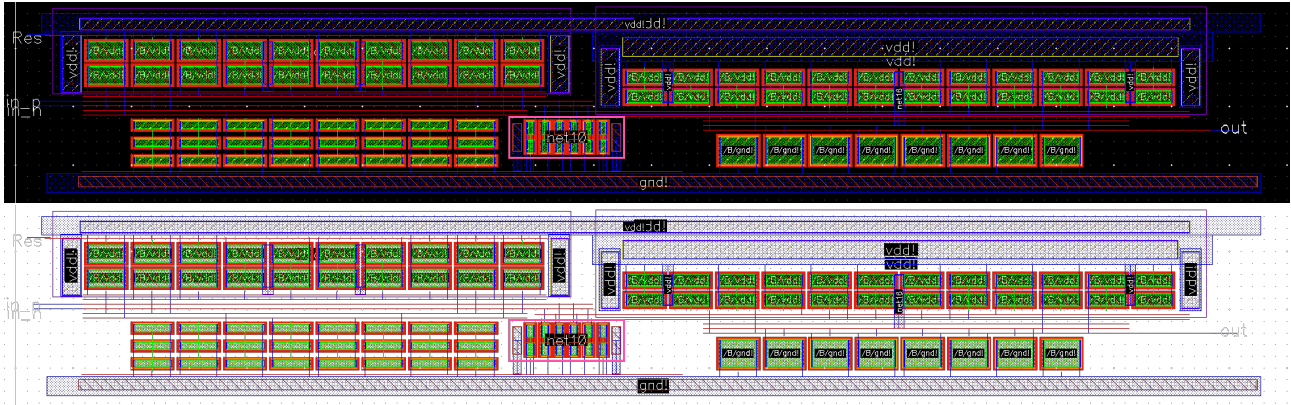


Figure 15: The full OTA layout

 


Figure 16: The partial OTA layouts

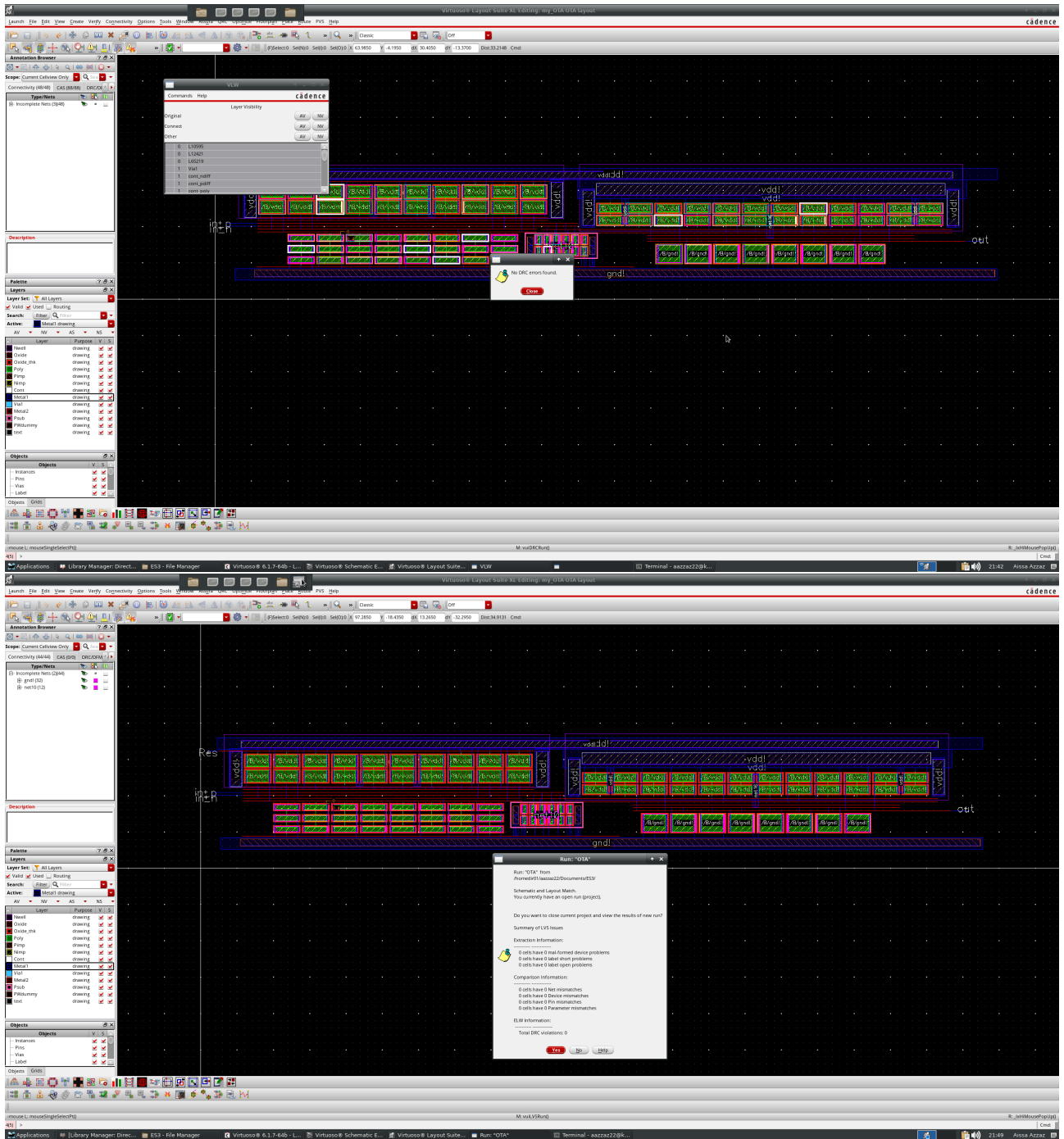


Figure 17: DRC and LVS results of the OTA layout

5. Layout Simulations

In the subsections bellow, the simulation results of schematic with the parasitics extracted from the layout are shown. The same test benches of the schematic simulations were used.

5.1 AC Response

AC Response

 


Figure 18: AC response of the OTA with the extracted parasitics

5.2 Step Response

 


Figure 19: Step response of the OTA with the extracted parasitics

6. Comparison

Table 3 shows the AC and step response for both simulation as well as Figures 20 and 21.

In this OTA including the extracted parasitics in the simulation resulted in slightly better f_t and SR . Overall, the both results for when including the parasitics or ignoring them are almost identical.

Table 3: The results of all the simulations

	Results without parasitics	Results with parasitics
f_{ta}	11.56908 MHz	11.59242 MHz
BW	123.163 kHz	127.6024 kHz
A_0	39.48111 dB	39.48111 dB
PM	75.3938°	75.4154°
Slew Rate	14.334105 MV/s	14.994513 MV/s

AC Response

 


Figure 20: Comparison of the AC response of the OTA with and without the extracted parasitics

 


Figure 21: Comparison of the step response of the OTA with and without the extracted parasitics