



CREATE OUTPUT MATCHING NETWORK USING TLs

With the input matching network in place, the output of the amplifier is matched to 50 Ohms.

1) The input reflection of "S11" is set to the complex conjugate of the impedance to be matched to 50Ohms (in this case, "Opt", the optimum noise match).

2) The TLout1 and TLout2 lengths are optimized until the a perfect matching happens between load and the matching network i.e. until $\text{mag}(S(1,1))=0$.

SIMULATIONS

S-PARAMETERS

SP1

Freq=2 GHz

S-parameter simulation is run at a single frequency (2GHz).

GOAL

Goal

Γ_{out}

$\text{Expr}=\text{"mag}(S(1,1))"$

SimInstanceName="SP1"

Weight=1

LimitName[1]="mag_S11"

LimitType[1]="Inside"

LimitMin[1]=0

LimitMax[1]=0.0001

LimitWeight[1]=1

OPTIM

Optim1

OptimType=Gradient

ErrorForm=L2

MaxIters=25

DesiredError=0.0

StatusLevel=2

FinalAnalysis="None"

NormalizeGoals=no

SetBestValues=yes

SaveSols=yes

SaveGoals=yes

SaveOptimVars=yes

UpdateDataset=yes

SaveNominal=yes

SaveAllIterations=no

UseAllOptVars=yes

UseAllGoals=yes

SaveCurrentEF=no

EnableCockpit=yes

SaveAllTrials=no