



## CREATE OUTPUT MATCHING NETWORK: Step 1

With the input matching network in place, the output of the amplifier is matched to 50 Ohms.

- 1) The reflection coefficient of the complete amplifier (input matching network, device, stabilizing network) is measured, with a shunt inductor at the output.
- 2) The inductor is swept until the real part of the amplifier's output impedance is 50 Ohms (see OutputMatch.dds).

### SIMULATIONS

S-PARAMETERS	PARAMETER SWEEP
 S_Param SP1 Freq=2 GHz	 ParamSweep Sweep1 SweepVar="L_value" SimInstanceName[1]="SP1" SimInstanceName[2]= SimInstanceName[3]= SimInstanceName[4]= SimInstanceName[5]= SimInstanceName[6]= Start=6.4 Stop=7.2 Step=0.1

S-parameter simulation is run at a single frequency 2GHz), while the inductor value is swept.

### VARIABLES

Var VAR  
Eqn VAR1  
L\_value=0

"L\_value" is defined here and set to 0. The actual values used in simulation are set in the ParamSweep component.

